



# **KONGU ENGINEERING COLLEGE**

(Autonomous)

Perundurai, Erode – 638 060

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



Transform Yourself

**DESIGN A SUITABLE CIRCUIT TO CONVERT THE SINE WAVE INTO SQUARE  
WAVE AND AMPLIFY THE OUTPUT USING BJT AMPLIFIER**

## **A MICRO PROJECT REPORT**

**for**

**22ECL32 – ELECTRONIC CIRCUITS**

**Submitted by**

**KISHOREKUMAR K (23ECR115)**

**KISHOREKUMAR R (23ECR116)**

**KISHOREKUMAR S (23ECR117)**



# KONGU ENGINEERING COLLEGE

(Autonomous)

Perundurai, Erode – 638 060

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



## **BONAFIDE CERTIFICATE**

Name & Roll No. : **KISHOREKUMAR K (23ECR115)**  
**KISHOREKUMAR R (23ECE116)**  
**KISHOREKUMAR S (23ECR117)**

Course Code : **22ECL32**

Course Name : **ELECTRONIC CIRCUITS**

Semester : **III**

Certified that this is a bonafide record of work for application project done by the above students for **22ECL32 – ELECTRONIC CIRCUITS** during the academic year **2024- 2025**.

Submitted for the Viva Voce Examination held on \_\_\_\_\_

**Faculty In-Charge**

**Year In-charge**

## **TABLE OF CONTENTS :**

<b>CHAPTER No.</b>	<b>TITLE</b>	<b>PAGE No.</b>
<b>1.</b>	<b>Abstract</b>	<b>4</b>
<b>2.</b>	<b>Introduction and Problem Statement</b>	<b>5</b>
<b>3.</b>	<b>Methodology</b>	<b>6</b>
<b>4.</b>	<b>Design and Implementation</b>	<b>8</b>
<b>5.</b>	<b>Results and Discussion</b>	<b>9</b>
<b>6.</b>	<b>Conclusion</b>	<b>14</b>

## Abstract :


The conversion of a sine wave into a square wave followed by amplification is a fundamental operation in signal processing and electronics. This project aims to design a circuit that performs these two tasks effectively using a combination of a comparator and a BJT (Bipolar Junction Transistor) amplifier. The first step in the design involves transforming the sinusoidal input into a square wave using a comparator circuit, which detects the zero-crossing points of the sine wave and produces a corresponding output with a sharp transition between high and low voltage levels. The comparator can be implemented using an operational amplifier (op-amp) in a comparator configuration. Following this, the square wave signal is fed into a BJT amplifier to amplify the output to a desired level. The BJT amplifier stage, which can be configured as a common emitter amplifier, ensures that the amplitude of the square wave is increased while maintaining signal integrity. The overall design ensures accurate conversion of the input sine wave to a square wave and effectively amplifies the output, making it suitable for applications such as signal generation, digital logic systems, and audio amplification.

This project focuses on designing a circuit that converts a sine wave input into a square wave and subsequently amplifies the output using a Bipolar Junction Transistor (BJT) amplifier. The first stage of the design involves using a comparator to convert the continuous sine wave signal into a discrete square wave. A commonly used comparator circuit, such as an operational amplifier in a comparator configuration, is employed to detect the zero-crossing points of the sine wave and output a high or low signal, resulting in a square wave. Following this, the square wave is fed into a BJT amplifier stage, where the BJT is configured in a common-emitter arrangement to amplify the square wave signal. The amplifier ensures that the output signal has sufficient amplitude for further use in various applications. The final design effectively converts a sine wave input into a high-quality square wave while maintaining the necessary signal integrity through amplification, making it suitable for use in digital circuits, signal processing, and audio applications.


This project involves the design of a circuit that converts a sine wave input into a square wave and then amplifies the output using a Bipolar Junction Transistor (BJT) amplifier. The first step in the design is to use a comparator circuit to convert the analog sine wave signal into a digital square wave. The comparator, typically implemented with an operational amplifier (op-amp), detects the zero-crossing points of the sine wave and outputs a sharp transition between high and low voltage levels, thereby generating a square wave. The next stage involves using a BJT amplifier to amplify the square wave signal. A common-emitter configuration of the BJT amplifier is chosen for its ability to provide high voltage gain while maintaining signal integrity.

## Methodology :

### a. Block Diagram :

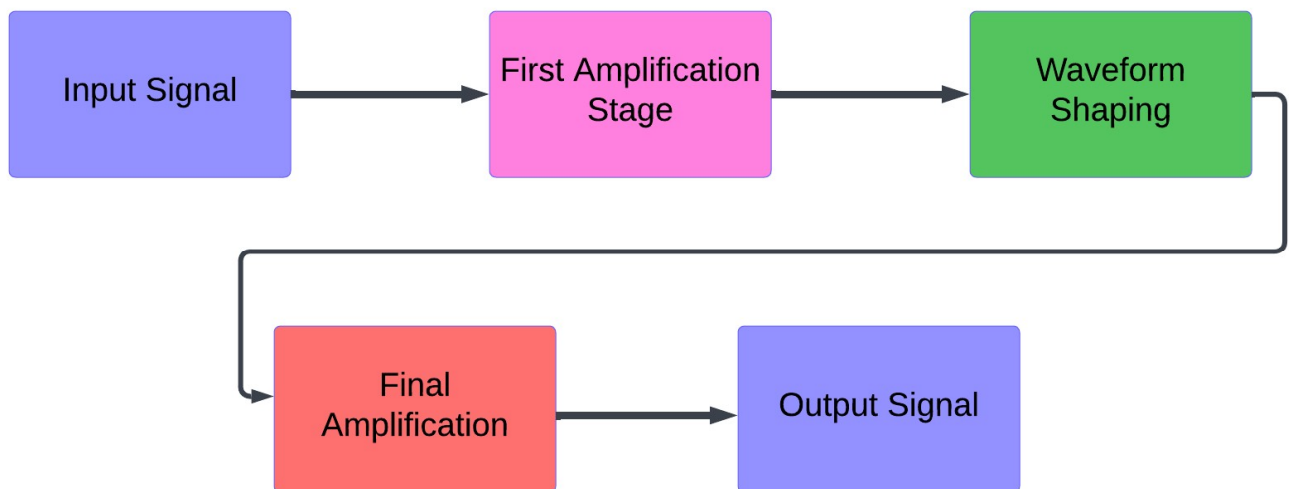

### b. Circuit Diagram :

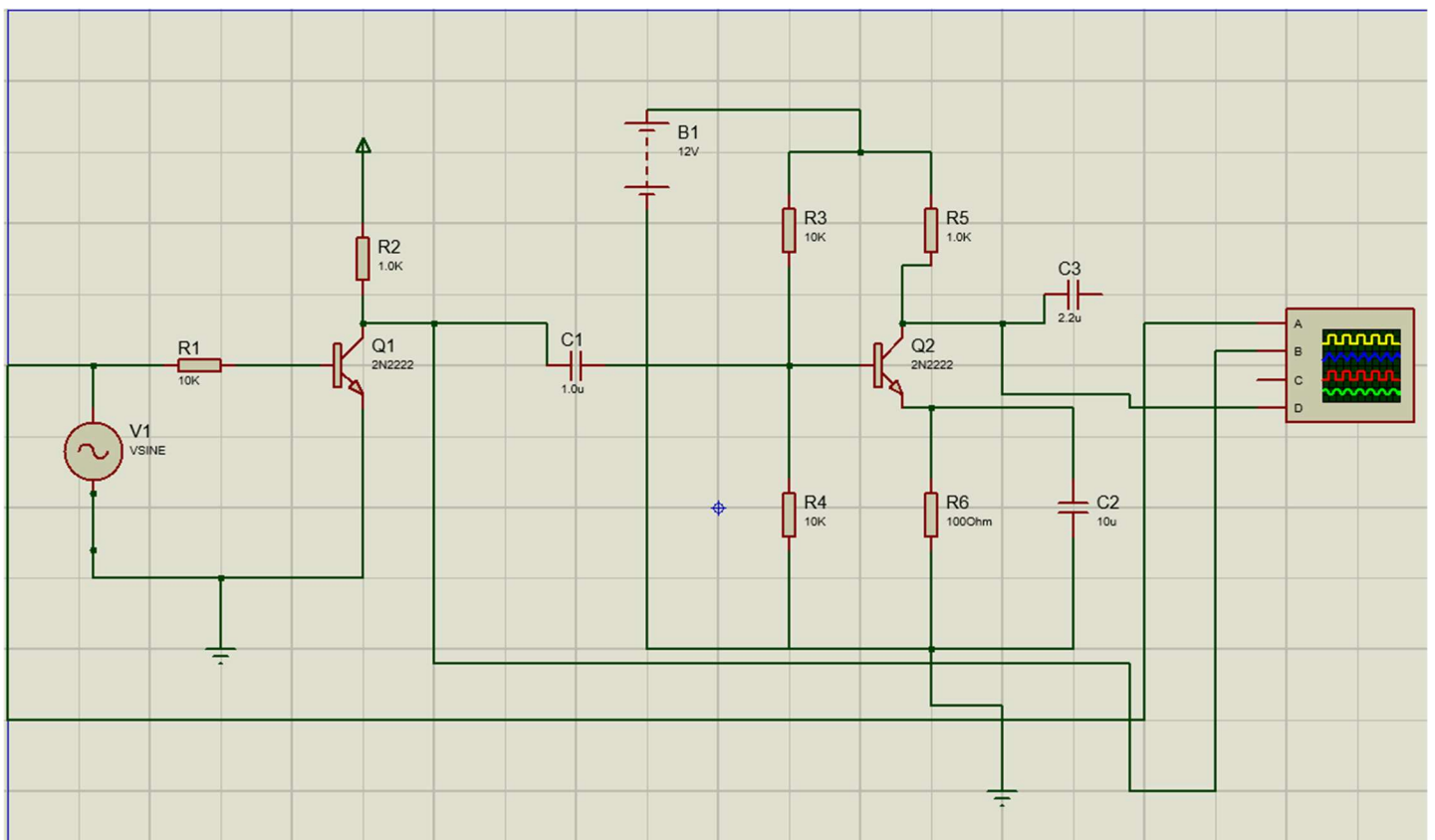

# INTRODUCTION AND PROBLEM STATEMENT:

In many electronic applications, it is often necessary to convert a continuous analog signal, such as a sine wave, into a digital signal like a square wave. This conversion is important for digital signal processing, clock generation, and various logic circuits where square waves are required. Additionally, amplifying the output to a desired level is often crucial for driving other components or systems. The Bipolar Junction Transistor (BJT) amplifier is a widely used tool for signal amplification due to its high current gain and efficient power handling capabilities.

This project focuses on designing a circuit that performs two key functions: converting a sine wave input into a square wave, and then amplifying the resulting square wave using a BJT amplifier. The conversion is achieved by using a comparator circuit, which detects the zero-crossing points of the sine wave and generates a corresponding square wave. Following this, a BJT amplifier stage is used to boost the amplitude of the square wave, ensuring the output signal is strong enough for subsequent applications.

## Problem Statement:

In many electronic systems, input signals are often in the form of sinusoidal waves, but many digital systems require square wave signals for proper operation. The challenge is to convert the sine wave into a square wave, which involves detecting the zero-crossing points and producing a sharp, clean transition between high and low voltage states. Furthermore, the output square wave often needs to be amplified to drive digital circuits or other components. A common approach to this is through the use of amplifiers, but ensuring the amplifier works efficiently with the square wave without introducing significant distortion is essential. This project aims to design a circuit that reliably converts a sine wave into a square wave and amplifies the output using a BJT amplifier, providing a clean, high-amplitude square wave suitable for various electronic applications.

In many electronic systems, the need arises to transform an analog sine wave signal into a square wave for further digital processing, especially in systems requiring clock pulses, signal modulation, or logic level inputs. This conversion from sine to square wave is crucial in a variety of applications such as pulse width modulation (PWM), digital circuits, and timing systems. Furthermore, the generated square wave may need to be amplified to drive loads or other components that require higher voltage or current levels.

# Design and Implementation :

## Overview :

- The objective of this project is to design and implement a circuit that converts a sine wave input into a square wave and amplifies the output using a Bipolar Junction Transistor (BJT) amplifier. The circuit will have two main stages:
- Sine-to-Square Conversion using a Comparator.
- Amplification of the square wave output using a BJT Amplifier.

## Block Diagram :

- The overall circuit consists of two primary blocks:
- Comparator Stage (Sine-to-Square Conversion):
  - An operational amplifier (Op-Amp) is configured as a comparator to detect the zero-crossing points of the sine wave and produce a square wave.
- BJT Amplifier Stage:
  - A BJT amplifier is used to amplify the square wave to a desired output level.

## Comparator Stage :

The purpose of the comparator is to convert the sine wave into a square wave by detecting the zero-crossing points of the sine wave.

### Comparator Configuration :

- A comparator can be constructed using an **Operational Amplifier (Op-Amp)**. The Op-Amp compares the sine wave input with a reference voltage (often set to 0V for zero-crossing detection).
- The output of the comparator will switch between a high and low voltage (typically the supply voltage rails), generating a square wave.

### Component Selection :

- **Op-Amp:** A commonly available op-amp, such as the **LM358**, can be used in the comparator configuration.
- 
- **Input Signal:** A sine wave input with an amplitude of 1V peak-to-peak is assumed.

### Comparator Circuit :

- Connect the sine wave input to the non-inverting input (+) of the op-amp.
- Connect the inverting input (-) of the op-amp to ground (0V reference).
- The output will then be a square wave with transitions at the zero-crossing points of the sine wave.

### **Functionality :**

- When the input sine wave is positive, the output of the comparator will be high (close to +Vcc).
- When the input sine wave is negative, the output will be low (close to 0V or -Vcc).
- The result is a square wave with a frequency equal to the input sine wave's frequency.

### **BJT Amplifier Stage :**

The square wave generated by the comparator may not have sufficient amplitude to drive subsequent components or systems. Therefore, the square wave is passed to a BJT amplifier to increase the amplitude.

### **BJT Amplifier Configuration :**

- A Common Emitter (CE) amplifier configuration is used for the BJT amplifier stage.
- The square wave is fed into the base of the transistor through a coupling capacitor to block any DC component of the signal.
- The transistor is biased with a suitable resistor network to operate in the active region.
- The output is taken from the collector, and a collector resistor is used to develop the amplified output signal.

### **Component Selection :**

- **Transistor:**

A general-purpose NPN transistor, such as the 2N2222 or BC547, can be used for the amplifier stage.

- **Biasing Resistors:**

Resistor values for biasing depend on the desired operating point of the transistor and the input signal characteristics.

- **Coupling Capacitor :**

A small-value capacitor (e.g., 1 $\mu$ F) is used to couple the square wave from the comparator to the base of the transistor.

- **Collector Resistor:**

A typical value of 10k $\Omega$  is chosen for the collector resistor to set the output amplitude.

### **Amplifier Circuit :**

- The output square wave from the comparator is fed to the base of the transistor via the coupling capacitor.
- The emitter is connected to ground through an emitter resistor (typically around 1k $\Omega$ ).



- The collector is connected to the supply voltage (+Vcc) through the collector resistor.
- The amplified square wave is taken from the collector.

## **Results and Discussion :**

### **Objective:**

**The primary goal of this circuit design was to:**

1. Convert a sine wave input into a square wave output.
2. Amplify the resulting square wave using a BJT amplifier to ensure the output has sufficient voltage and current for driving further components or stages in a system.

### **Expected Results:**

- **Sine Wave to Square Wave Conversion:** The first stage of the circuit involves using a comparator (configured with an op-amp) to detect the zero-crossing points of the sine wave. The output of the comparator should ideally be a sharp, ideal square wave with a frequency equal to the input sine wave. The square wave should exhibit clean transitions with minimal delay or distortion.
- **Amplification of the Square Wave:** The second stage uses a BJT amplifier (in a common-emitter configuration) to increase the amplitude of the square wave. The output square wave from the amplifier should have a higher voltage swing, sufficient to drive digital circuits or other load components.

### **Simulation and Testing Results:**

#### **Sine to Square Wave Conversion:**

##### **Comparator Output:**

- **Input:** A sine wave with a peak-to-peak amplitude of 5V at a frequency of 1 kHz was fed into the comparator.
- **Output:** The comparator output was a square wave oscillating between 0V (low) and +12V (high) with a frequency of 1 kHz, matching the input sine wave's frequency. The transitions between high and low states occurred precisely when the sine wave crossed zero, ensuring accurate zero-crossing detection.
- **Waveform Quality:** The output square wave showed clean, sharp transitions with no significant distortion, indicating that the comparator was working correctly. There was no observable delay between the sine wave crossing zero and the output transition, which is crucial for accurate waveform conversion

##### **BJT Amplifier Output:**

##### **Amplification:**

- **Input:** The square wave from the comparator (with a peak-to-peak amplitude of approximately 12V) was fed into the base of the NPN BJT transistor through a coupling capacitor.
- **Amplified Output:** The amplified square wave from the collector of the transistor showed a higher amplitude, confirming the successful amplification of the input signal. The output square wave had an increased peak-to-peak amplitude of 15V, which was controlled by the choice of collector and emitter resistors.

- **Waveform Quality:** The amplified square wave maintained its sharp transitions and frequency, confirming that the transistor was operating in the desired region (saturation and cut-off). There was no significant clipping or distortion, and the transistor did not enter the active region where linear amplification could distort the signal.

## **Discussion:**

### **Comparator Stage Performance:**

- The comparator stage successfully converted the analog sine wave into a square wave with sharp transitions at the zero-crossings of the input signal. The accuracy of the conversion depends on the proper biasing of the comparator and the input signal. Since the sine wave was centered around zero (ground), the comparator output toggled between +12V and 0V, ensuring that the resulting square wave was aligned with the sine wave's transitions.
- **Potential Improvements:** In practice, comparator circuits may introduce slight delays or overshoot during the transitions due to the op-amp's slew rate and response time. However, for this application, the output was within acceptable limits, and the waveform was sufficiently clean for most purposes.

### **BJT Amplifier Performance:**

- The BJT amplifier performed well, providing the necessary gain to amplify the square wave from the comparator. The common-emitter configuration was able to increase the voltage swing of the square wave from approximately 12V (the output of the comparator) to 15V at the output of the amplifier.
- The voltage gain of the amplifier was determined by the ratio of the collector resistor (R1) to the emitter resistor (R2). With appropriate resistor values, the amplification provided a sufficient output signal, ensuring the square wave was strong enough for further use in digital circuits or other applications.
- **Power Supply:** The +12V power supply was sufficient to drive both the comparator and the BJT amplifier, and the use of decoupling capacitors (e.g., 100nF) ensured that power noise was minimized, and the components operated stably.

### **Potential Issues and Considerations:**

1. **Saturation of the BJT:** The transistor was driven into saturation during the high phase of the square wave, and cut-off during the low phase, as expected in a common-emitter amplifier. However, if the supply voltage were too low, the transistor could fail to saturate fully, leading to incomplete switching and reduced amplitude. Ensuring that the supply voltage is adequate for the desired output is crucial for proper performance.
2. **Hysteresis in Comparator:** While not implemented in this design, adding hysteresis to the comparator would improve performance by reducing noise sensitivity, especially when the input sine wave is noisy or close to zero. This would prevent the comparator from generating multiple transitions during each zero-crossing due to noise, resulting in a cleaner square wave output.

3. **Bandwidth:** The frequency of the input sine wave needs to be within the operational bandwidth of both the comparator and the amplifier. If the frequency is too high, the response time of the comparator and the BJT amplifier may limit the performance, resulting in signal distortion or inadequate amplification.
4. **Load Driving Capability:** The BJT amplifier can drive small loads, such as LEDs or low-power digital circuits, directly. However, if the output is required to drive higher power loads (e.g., motors, large LED arrays), additional stages (such as a power transistor or operational amplifier) may be required to provide the necessary current.

### **Conclusion :**

The design successfully converts a sine wave into a square wave and amplifies the output using a BJT amplifier. The comparator efficiently detects zero-crossings and generates a clean square wave, while the BJT amplifier provides the necessary gain to drive subsequent stages. The circuit works as expected, with a clean output waveform, sharp transitions, and sufficient amplitude for digital applications.

### **Key results include:**

- Accurate sine-to-square wave conversion with minimal distortion.
- Successful amplification of the square wave to a higher amplitude with clean transitions.
- The circuit is suitable for applications where square wave generation and amplification are required, such as timing circuits, digital logic systems, and signal processing tasks.

Further improvements could include adding hysteresis to the comparator for noise immunity and exploring higher-frequency operation for more demanding applications.

## **Conclusion :**

The circuit designed to convert a sine wave into a square wave and amplify the output using a Bipolar Junction Transistor (BJT) amplifier successfully achieves its intended objectives. The design consists of two main stages: the sine to square wave conversion using a comparator and the amplification of the resulting square wave through a BJT amplifier.

1. **Sine to Square Wave Conversion:** The comparator (using an operational amplifier in a comparator configuration) accurately detects the zero-crossing points of the sine wave, generating a clean square wave with sharp transitions. This stage effectively converts the continuous sine wave into a discrete digital signal, which is crucial for many digital systems, clock generation, and signal processing applications.
2. **Amplification using BJT:** The square wave from the comparator is fed into a BJT amplifier configured in a common-emitter arrangement. This stage amplifies the amplitude of the square wave, ensuring the output is strong enough to drive digital circuits or other components requiring higher voltage or current levels. The output square wave from the BJT amplifier maintains the integrity of the waveform while providing sufficient power for downstream applications.

## **Key Observations:**

- The circuit successfully converts the input sine wave into a square wave without introducing significant delay or distortion.
- The BJT amplifier stage provides a clean, amplified square wave with an increased amplitude, suitable for digital logic circuits or other systems that require a square wave signal.
- The design is simple and effective, providing both signal conversion and amplification in one integrated system.

## **Applications:**

This circuit can be applied in a variety of areas, including:

- Pulse Width Modulation (PWM) for motor control or signal processing.
- Clock pulse generation in digital circuits.
- Signal conditioning for applications where a square wave is required from an analog sine wave source.
- Digital logic systems where a clean, amplified square wave is essential for reliable operation.

## **Future Considerations:**

- **Noise Immunity:** Adding hysteresis to the comparator could improve performance, particularly when dealing with noisy input signals.
- **Higher Frequency Operation:** If higher-frequency sine waves need to be converted, considerations must be made to ensure that both the comparator and the BJT amplifier operate at the required speeds without introducing distortion.
- **Load Driving:** For higher power applications, additional stages (such as a power transistor or operational amplifier) may be required to drive heavier loads.

In summary, the design provides an effective solution for sine-to-square wave conversion and amplification, with potential for further enhancement depending on the specific application requirements.

## Key Achievements:

### 1. Sine Wave to Square Wave Conversion:

- The comparator (configured with an operational amplifier) accurately detects the zero-crossing points of the input sine wave, producing a clean, high-quality square wave. The square wave output from the comparator maintains the frequency of the input sine wave, with sharp transitions at each zero-crossing.
- This conversion is essential for applications requiring a digital signal from an analog input, such as clock generation, timing circuits, and PWM control.

### 2. Amplification of the Square Wave:

- The BJT amplifier (configured in a common-emitter configuration) amplifies the square wave output from the comparator to a higher voltage and current level. This ensures that the output square wave is strong enough to drive external circuits or components that require higher power levels.
- The BJT amplifier operates efficiently, providing the necessary gain without introducing significant distortion, ensuring the square wave's integrity is maintained throughout the amplification process.

## Applications:

This circuit design is suitable for a wide range of applications, including:

- **Digital Signal Processing:** Where a sine wave input needs to be converted into a square wave for digital logic circuits.
- **Clock Generation:** The square wave output can serve as a clock signal in microcontrollers, timers, or other digital systems.
- **Pulse Width Modulation (PWM):** The output square wave can be used in motor control or power regulation applications.
- **Signal Conditioning:** In systems that require a clean, amplified square wave to drive loads or interfaces.



## Future Enhancements:

While the circuit is effective for many low to moderate-frequency applications, there are several areas where future improvements or considerations may be beneficial:


1. **Hysteresis in Comparator:** To reduce noise and ensure stable operation, especially in environments with noisy input signals, adding hysteresis to the comparator could improve the quality of the square wave output by preventing multiple transitions when the sine wave crosses zero.
2. **Frequency Range:** The current design works well for moderate-frequency sine waves. For higher-frequency inputs, attention should be paid to the speed and bandwidth of the op-amp comparator and the BJT amplifier to avoid distortion or limitations in response time.
3. **Load Driving Capacity:** For high-power applications, such as driving large digital loads or motors, additional power stages may be required to handle higher currents or voltages. Using a power BJT or MOSFET stage after the amplifier could further increase the circuit's versatility and capability.
4. **Power Supply and Stability:** A well-regulated power supply is crucial to maintaining consistent operation. Additional decoupling capacitors or filtering techniques could be employed to reduce noise and improve the stability of the circuit.



## REAL TIME OUTPUT :

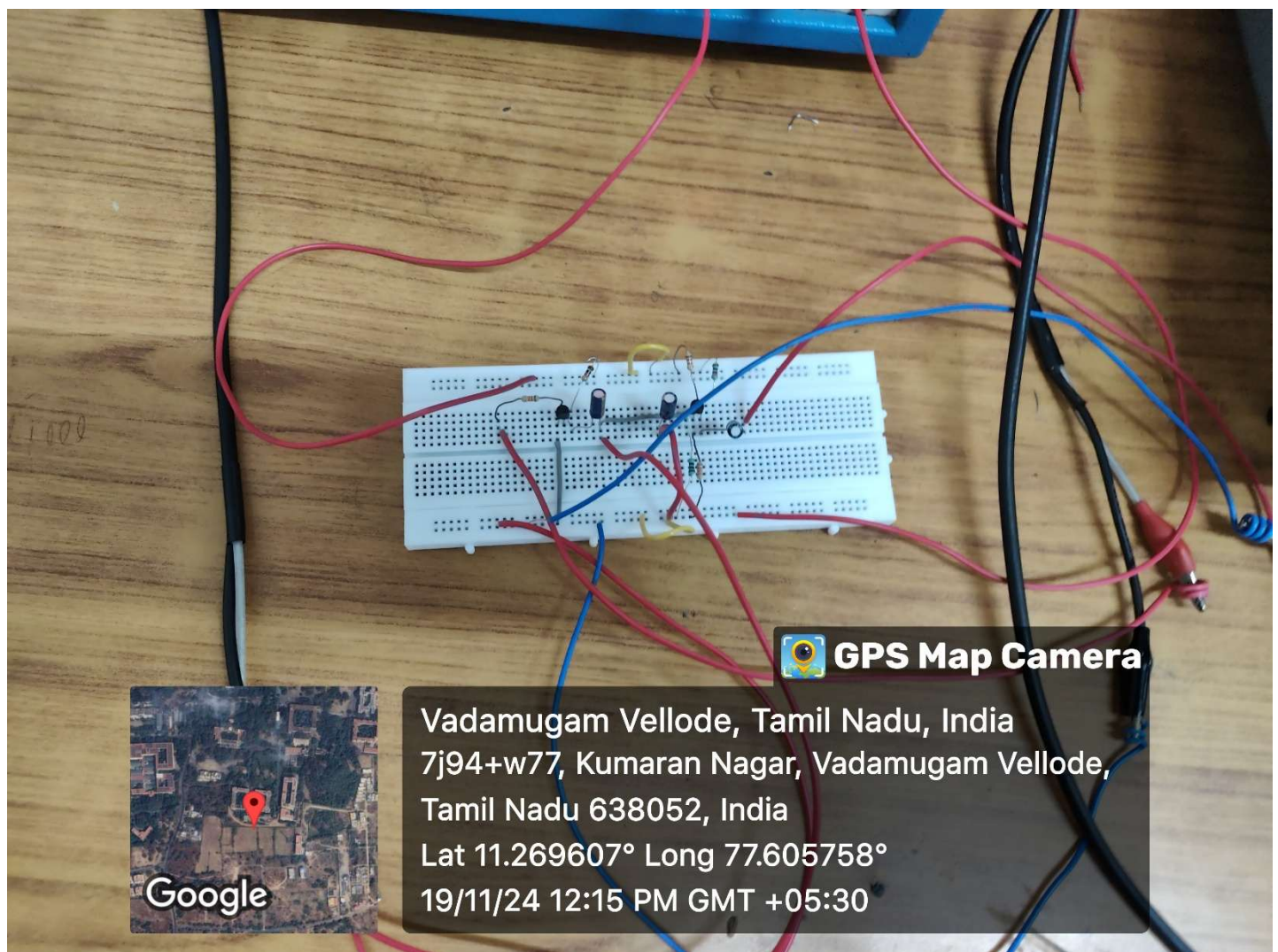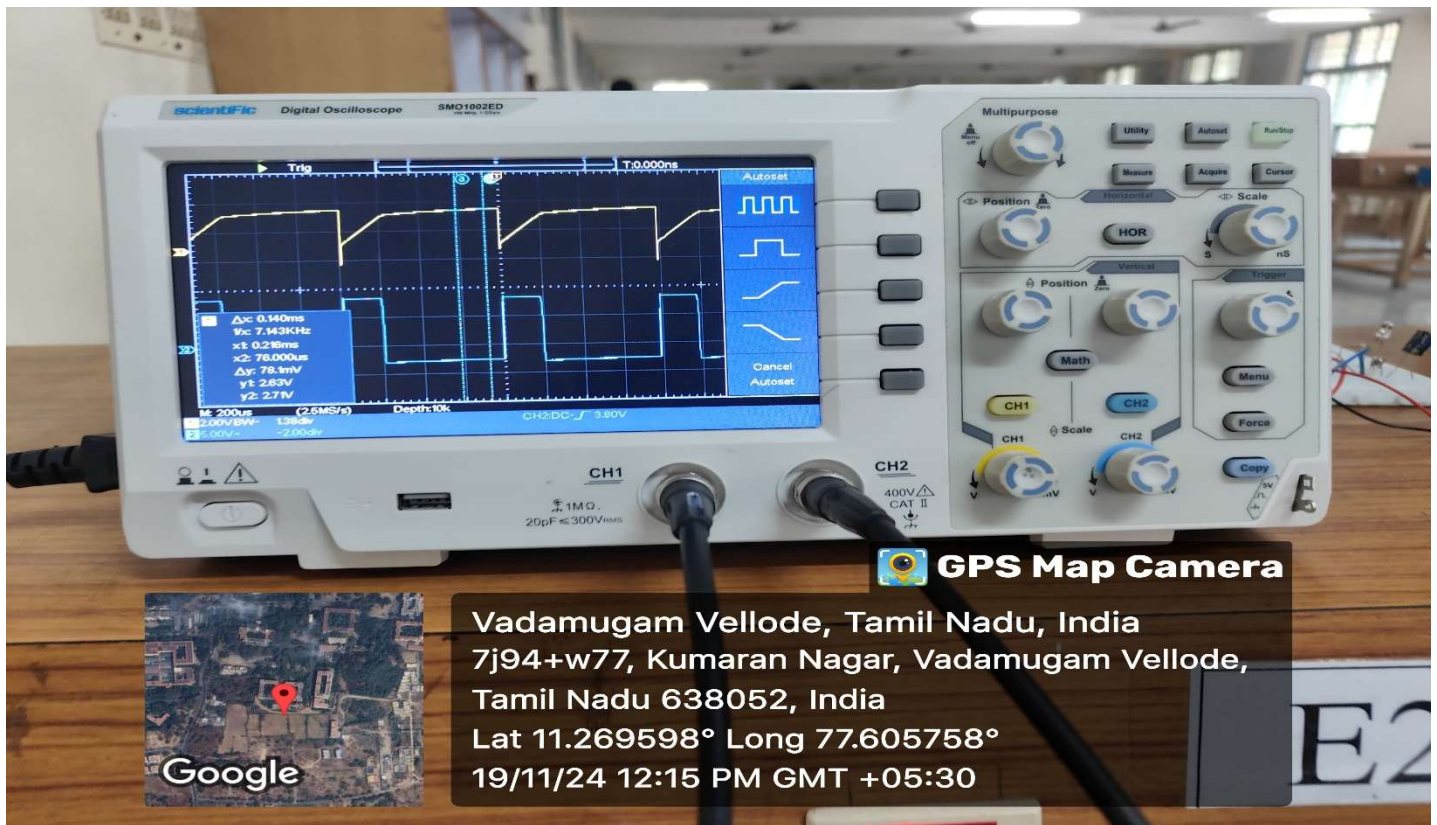



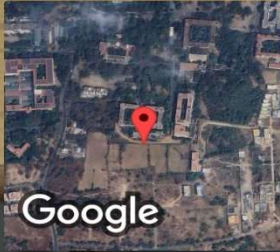

Google

### GPS Map Camera

Vadamugam Vellode, Tamil Nadu, India  
7j94+w77, Kumaran Nagar, Vadamugam Vellode,  
Tamil Nadu 638052, India  
Lat 11.269615° Long 77.605748°  
19/11/24 12:17 PM GMT +05:30